

Control Systems

G V V Sharma*

CONTENTS

1 Feedback Circuits 1

Abstract—This manual is an introduction to control systems based on GATE problems. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/codes>

1 FEEDBACK CIRCUITS

1.0.1. An amplifier having a low-frequency gain of 1000 and poles at 10^4 Hz and 10^5 Hz is operated in a closed negative-feedback loop with a frequency-independent β .

(a) For what value of H do the closed-loop poles become coincident? At what frequency?
(b) What is the low-frequency gain corresponding to the situation in (a)? What is the value of the closed-loop gain at the frequency of the coincident poles?

(c) What is the value of Q corresponding to the situation in (a)?

(d) If H is increased by a factor of 10, what are the new pole locations? What is the corresponding pole Q?

Solution: Given, low frequency Gain and two poles. Therefore, $G(s)$ can be written as..,

$$G(s) = \frac{G_0}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)} \quad (1.0.1.1)$$

where, $-p_1$ and $-p_2$ are poles of $G(s)$. Parameters given are shown in Table.1.0.1:1

$$G_0 = 1000 \quad (1.0.1.2)$$

$$\text{Therefore, } G(s) = \frac{1000}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)} \quad (1.0.1.3)$$

Parameter	Value
Low Frequency Gain	1000
Pole 1 (p_1)	10^4 Hz
Pole 2 (p_2)	10^5 Hz

TABLE 1.0.1: 1

Where p_1 and p_2 are

$$p_1 = 2\pi 10^4 \text{ rad/sec} \quad (1.0.1.4)$$

$$p_2 = 2\pi 10^5 \text{ rad/sec} \quad (1.0.1.5)$$

Now, we connect the system in a negative feedback of feedback factor H. We know that the closed loop gain of a negative feedback system is.,

$$T(s) = \frac{G(s)}{1 + G(s)H} \quad (1.0.1.6)$$

1.0.2. For what value of H do the closed-loop poles become coincident? At what frequency?

Solution: Given the negative feedback system, the closed loop transfer function is:

$$T(s) = \frac{\frac{G_0}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)}}{1 + \frac{HG_0}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)}} \quad (1.0.2.1)$$

$$(1.0.2.2)$$

$$T(s) = \frac{G_0}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right) + HG_0} \quad (1.0.2.3)$$

$$T(s) = \frac{G_0}{\frac{s^2}{p_1 p_2} + \left(\frac{1}{p_1} + \frac{1}{p_2}\right)s + HG_0} \quad (1.0.2.4)$$

$$(1.0.2.5)$$

For this equation to have equal and repetitive roots, $D=0$

$$b^2 - 4ac = 0 \quad (1.0.2.6)$$

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

$$\left(\frac{1}{p_1} + \frac{1}{p_2}\right)^2 = \frac{4}{p_1 p_2} (G_0 H + 1) \quad (1.0.2.7)$$

$$H = \frac{(p_1 - p_2)^2}{4G_0 p_1 p_2} \quad (1.0.2.8)$$

Value of H on plugging in values:

$$H = 0.002025 \quad (1.0.2.9)$$

Using this our final closed loop transfer function is:

$$T(s) = \frac{1000}{2.533 \times 10^{-11} s^2 + 1.750 \times 10^{-5} s + 3.025} \quad (1.0.2.10)$$

Verify the poles of above transfer function using python code.

codes/ee18btech11036/ee18btech11036_1.py

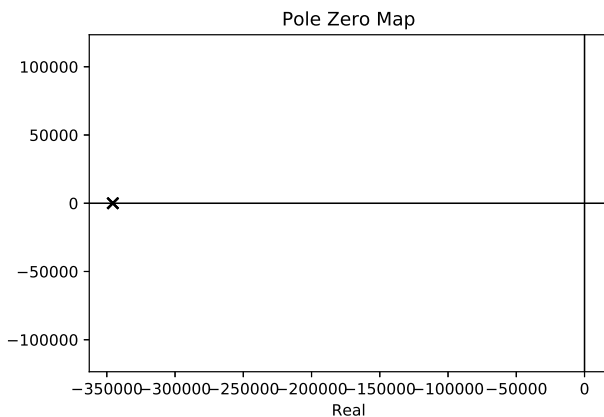


Fig. 1.0.2: 1

From the above graph is is evident that the system has two coinciding poles at frequency 345575.1 rad/sec

1.0.3. What is the low-frequency gain corresponding to the situation in (a)? What is the value of the closed-loop gain at the frequency of the coincident poles?

Solution: Putting $s=0$ in equation 1.0.2.10

$$\text{Gain} = \frac{1000}{3.025} \Rightarrow 330.578/50.378(\text{dB}) \quad (1.0.3.1)$$

$$(1.0.3.2)$$

Plot the transfer function above using the given code

codes/ee18btech11036/ee18btech11036_2.py

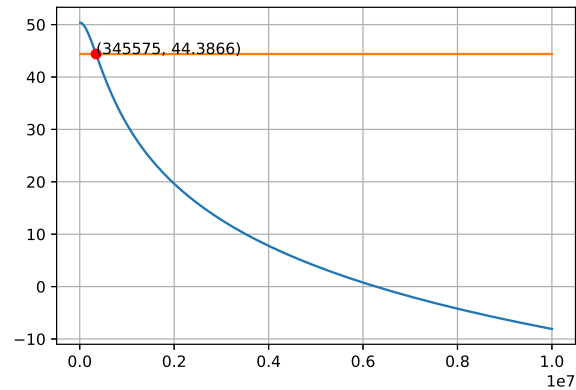


Fig. 1.0.3: 1

From the plot, the gain (dB) at pole frequency is 44.3866

1.0.4. What is the value of Q corresponding to the situation in(a)?

Solution:

In general, For a second order amplifier the C.E is.,

$$C.E = s^2 + 2\zeta\omega_n s + \omega_n^2 \quad (1.0.4.1)$$

The quality factor Q of equation.1.0.4.1, is given by

$$Q = \frac{1}{2\zeta} \quad (1.0.4.2)$$

From equation.1.0.2.5 and 1.0.1.5

$$\omega_n = \pm \sqrt{(HG_0 + 1) p_1 p_2} \quad (1.0.4.3)$$

$$\zeta = \pm \frac{2p_1 p_2}{\sqrt{(HG_0 + 1) p_1 p_2}} \quad (1.0.4.4)$$

Therefore, For the given second order amplifier with characteristic equation.1.0.2.6, the Q factor is,

$$Q = \pm \frac{\sqrt{(1 + HG_0) p_1 p_2}}{p_1 + p_2} \quad (1.0.4.5)$$

From equations 1.0.2.9, 1.0.1.5

$$Q = 0.5 \quad (1.0.4.6)$$

$$(1.0.4.7)$$

Parameter	Value
H	0.002025
Gain (0 freq)	50.378
Gain (pole freq)	44.38
Q	0.5

TABLE 1.0.4: 1

1.0.5. If H is increased by a factor of 10, what are the new pole locations? What is the corresponding pole Q?

Solution: H is increased by factor of 10, hence

$$H = 0.02025 \quad (1.0.5.1)$$

Using 1.0.2.5 we get :

$$T(s) = \frac{1000}{2.533 \times 10^{-11} s^2 + 1.750 \times 10^{-5} s + 21.25} \quad (1.0.5.2)$$

Find the poles of the given Tf using the following code:

```
codes/ee18btech11036/ee18btech11036_3.py
```

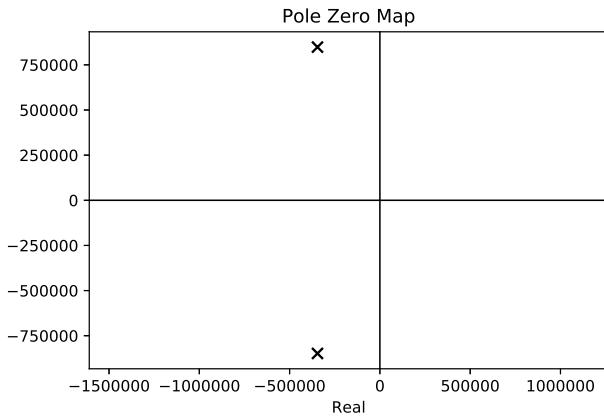


Fig. 1.0.5: 1

Poles are :

From equation 1.0.4.5

$$Q = \pm \frac{\sqrt{(1 + 10HG_0) p_1 p_2}}{p_1 + p_2} \quad (1.0.5.3)$$

Solving this we get :

$$Q = 1.325 \quad (1.0.5.4)$$

1.0.6. Find the step response of $T(s)$

Solution: The following code generates the desired response of in Fig. 1.0.3.

```
codes/ee18btech11036/ee18btech11036_4.py
```

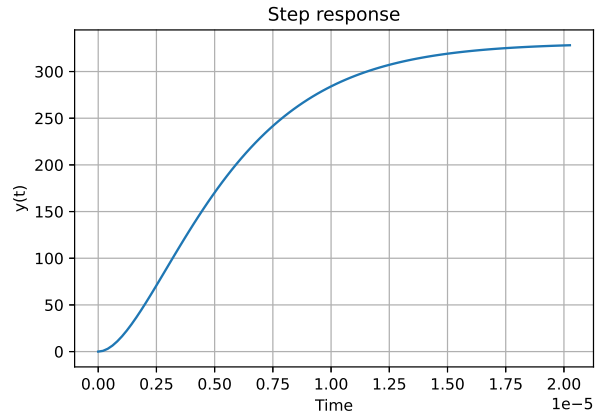


Fig. 1.0.6

1.0.7. Design a circuit that represents the transfer function 1.0.2.10

Solution: The circuit can be designed using an operational amplifiers having negative feedback. Consider the circuit shown in figure.1.0.7:1. Assume the gain of all the amplifiers are large. And assume no zero state response. Take the parameters in s-domain.

For the first amplifier., Applying KCL at

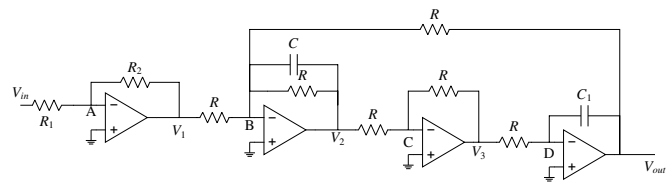


Fig. 1.0.7: 1

node A., Since, the opamp has large gain, potential at node A is assumed to be zero due to virtual short at node A.

$$\frac{0 - V_{in}(s)}{R_1} + \frac{0 - V_1(s)}{R_2} = 0 \quad (1.0.7.1)$$

$$\frac{V_{in}(s)}{R_1} = \frac{V_1(s)}{R_2} \quad (1.0.7.2)$$

$$\Rightarrow V_{in} = -\frac{V_1(s)R_1}{R_2} \quad (1.0.7.3)$$

For the second amplifier.., Applying KCL at node B.. Similarly potential at node B is zero.

$$\frac{-V_1(s)}{R} + \frac{-V_2(s)}{R} - sCV_2(s) + \frac{-V_{out}(s)}{R} = 0 \quad (1.0.7.4)$$

$$\frac{-V_1(s)}{R} + \frac{-V_2(s)}{R} - sCV_2(s) = \frac{V_{out}(s)}{R} \quad (1.0.7.5)$$

$$\frac{-V_1(s)}{R} = V_2(s) \left[sC + \frac{1}{R} \right] + \frac{V_{out}(s)}{R} \quad (1.0.7.6)$$

For the third amplifier.., Potential at node C is zero(Due to high gain of amplifier).Applying KCL at node C.

$$\frac{-V_2(s)}{R} + \frac{-V_3(s)}{R} = 0 \quad (1.0.7.7)$$

$$\Rightarrow V_2(s) = -V_3(s) \quad (1.0.7.8)$$

For the Fourth amplifier.., Potential at node D is zero.Applying KCL at node D.

$$\frac{-V_3(s)}{R} + sC_1(-V_{out}(s)) = 0 \quad (1.0.7.9)$$

$$V_3(s) = -sC_1RV_{out}(s) \quad (1.0.7.10)$$

From equation.1.0.7.10 and equation. 1.0.7.8..,

$$V_2(s) = sC_1RV_{out}(s) \quad (1.0.7.11)$$

Substituting the equation.1.0.7.6 and equation.1.0.7.11,

$$\frac{-V_1(s)}{R} = (s^2C_1CR + sC_1) V_{out}(s) + \frac{V_{out}(s)}{R} \quad (1.0.7.12)$$

$$V_1(s) = -(s^2C_1CR^2 + sC_1R + 1) V_{out}(s) \quad (1.0.7.13)$$

from equation.1.0.7.3 and equation.1.0.7.13.

$$V_1(s) = \frac{R_1}{R_2} (s^2C_1CR^2 + sC_1R + 1) V_{out}(s) \quad (1.0.7.14)$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_2}{R_1 (s^2C_1CR^2 + sC_1R + 1)} \quad (1.0.7.15)$$

Comparing equation.1.0.2.10 and

equation.1.0.7.15

$$R_2 = 33k\Omega \quad (1.0.7.16)$$

$$R_1 = 100\Omega \quad (1.0.7.17)$$

$$C_1CR^2 = 0.8373 \times 10^{-11} \quad (1.0.7.18)$$

$$C_1R = 0.5785 \times 10^{-5} F \quad (1.0.7.19)$$

$$\text{Let., } C_1 = 4nF \quad (1.0.7.20)$$

$$\Rightarrow C = 1nF \quad (1.0.7.21)$$

$$\text{and., } C_1R = 0.5785 \times 10^{-5} F \quad (1.0.7.22)$$

$$\Rightarrow R = 1.446k\Omega \quad (1.0.7.23)$$

Parameter	Value
R_1	100 Ω
R_2	33 k Ω
R	1.446 k Ω
C	1 nF
C_1	4 nF

TABLE 1.0.7: 1

From Table.1.0.7:1. The Final circuit is shown in figure.1.0.7

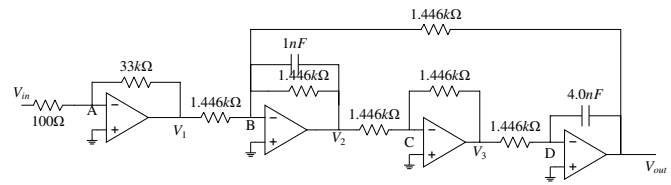


Fig. 1.0.7: 1

1.0.8. Verify the step response of the output from ngspice simulation.

Solution: The following netlist file does the transient analysis and store the Vout values with respect to time in a dat file.

```
codes/ee18btech11036/spice/ngspice_db.net
```

Following python code is to plot the step response.

```
codes/ee18btech11036/spice/
ee18btech11036_spice.py
```

The step response obtained is shown in the figure.1.0.8.The graph has steady state value equal to 50.3 dB.

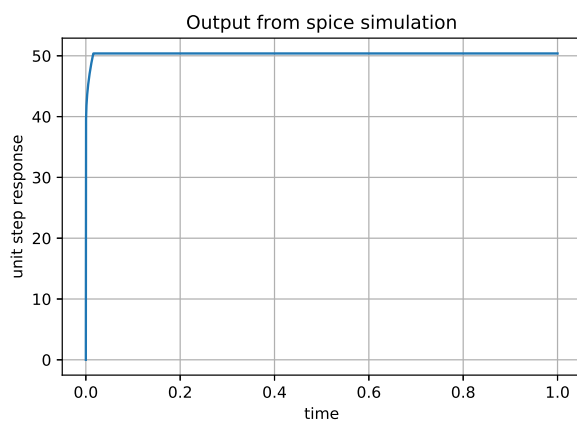


Fig. 1.0.8